

# High Current Power MOSFET with Current Mirror and Temperature Sense Diodes

*Using current mirror for current sensing in high current MOSFET applications significantly reduces power loss in current sensing circuit and lowers design cost by replacing expensive high power current sensors with inexpensive standard resistors.*

*Two temperature-sensing diodes monolithically integrated in the MOSFET's die monitor the junction temperature of the MOSFET, rather than that of the package or heat sink temperature. This significantly increases the precision of temperature measurement and reduces the protection gap for operating ambient temperature with minimal risk of damaging the device.*

*By Anatoliy Tsyrganovich, Leonid Neyman, and Abdus Sattar, IXYS Corporation*

IXYS MMIXT132N50P3 contains the current mirror to monitor the drain current in a major device and two diodes with common cathode utilizing the same die as the major device for temperature monitoring. The MMIXT132N50P3 symbol is shown in Figure 1 [1].

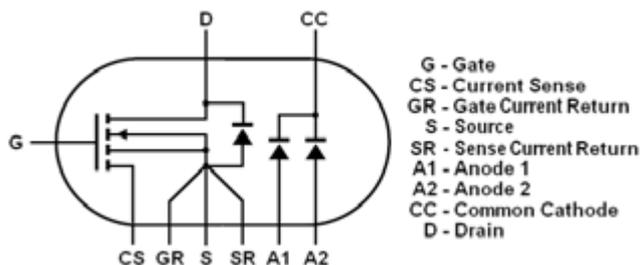


Figure 1: MMIXT132N50P3 Device Symbol

The current mirror is created as a part of the major MOSFET structure with common drain (D) and gate (G) terminals and separated source terminals (S and CS). To minimize errors related to the voltage drop on bounding wires from the source current of the major device, two separate terminals, one for a current mirror current return (SR) and the other for gate charge/discharge current (GR), are provided in the device. Temperature sensing diodes have separate terminals for anodes (A1, A2) and common cathode terminal (CC).

**Current Mirror Description**

The schematic diagram for the MMIXT132N50P3 current mirror is shown in Figure 2.

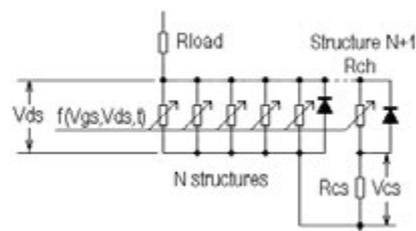


Figure 2: Current Mirror Schematic Diagram

As shown in Figure 2, MMIXT132N50P3 contains an N+1 identical structure with which N structures create the major MOSFET and the (N+1)th structure creates the current mirror. For this particular design, N = 200, and if no current sense resistor in the current mirror's source is used ( $R_{CS} = 0$ ), the current mirror's current is exactly 1/200 of the major device source current. There is no dependency on the MOSFET's drain/source voltage  $V_{DS}$ , and, as a result it is temperature-independent, providing measurements with maximum precision. However, if some sensor with finite resistance is used to convert current into voltage, the result of the measurement becomes  $V_{DS}$ -dependent because of the resistive divider created by the MOSFET's channel resistance  $R_{CH}$  and current sense resistor  $R_{CS}$ . This is especially important at low  $I_{DS}$  when drain/source voltage is low as well.

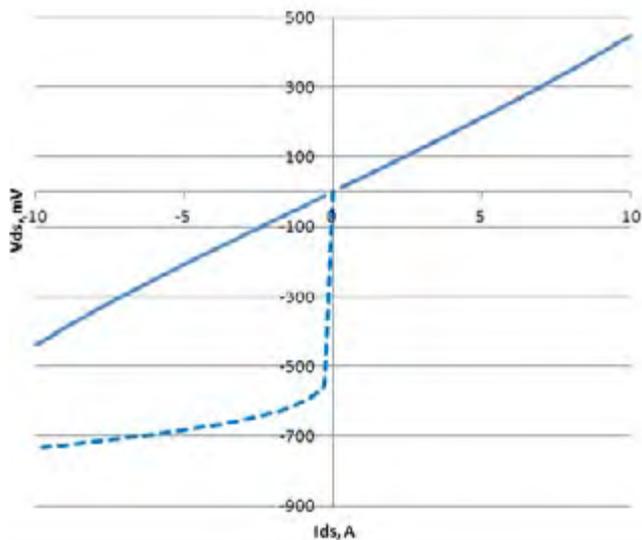


Figure 3:  $V_{DS}$  vs.  $I_{DS}$   
 Legend: Solid line - MOSFET is in ON state and channel is connected in parallel to the body diode Dashed line - MOSFET is in off state and body diode is conducting only

Figure 3 shows the MMIXT132N50P3 drain/source voltage drop ( $V_{DS}$ ) as a function of the drain/source current ( $I_{DS}$ ) at currents below 10 A, with currents flowing in both directions when drain is positive with respect to source (normal operations) and drain is negative with respect to source (inverse connection) with the MOSFET in ON and OFF states. If the MOSFET is in ON state,  $V_{DS}$  is described as  $V_{DS} = R_{DS(on)} * I_{DS}$  irrespective of  $I_{DS}$  polarity. If MOSFET is in OFF state and the body diode only sources current,  $V_{DS}$  is determined by the voltage drop across the body diode. Figure 4 shows a voltage drop across the current sense resistor ( $V_{CS}$ ) and Figure 5 represents the current through the current sense resistor at the same conditions as in Figure 3.

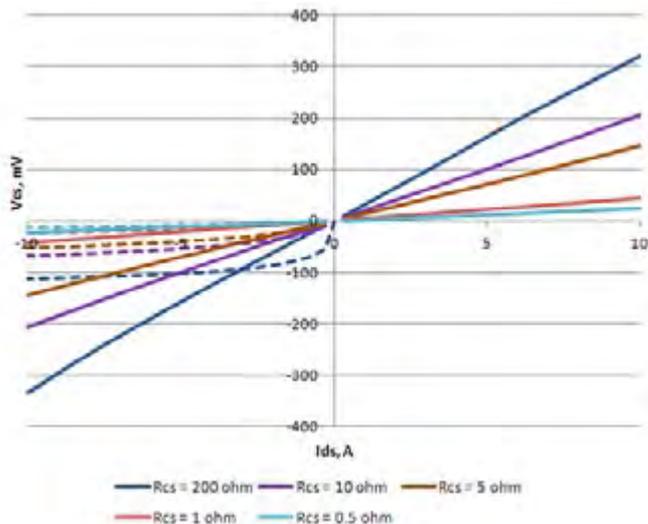


Figure 4:  $V_{CS}$  vs.  $I_{DS}$

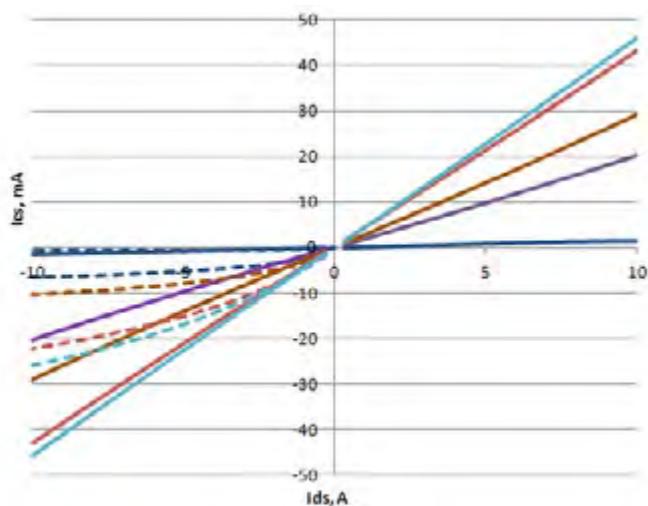


Figure 5:  $I_{CS}$  vs.  $I_{DS}$

Figures 4 and 5 clearly demonstrate that increasing current sense resistance  $R_{CS}$  increases  $V_{CS}$  but decreases  $I_{CS}$ . With  $R_{CS} = 0.5$  ohm,  $I_{CS}$  is close to the expected current mirror current, but  $V_{CS}$  is low. For example, at  $I_{DS} = 10$  A, expected  $I_{CS} = 10/200 = 0.05$  A, while actual  $I_{CS} = 46$  mA, while with  $R_{CS} = 200$  ohm,  $V_{CS}$  is close to  $V_{DS}$  (320 mV vs. 440 mV), but  $I_{DS}$  is only 1.57 mA, i.e. only 3.1% of the expected current. Figure 6 shows that it is a linear function between the current mirror's "head room", i.e. difference in voltage between  $V_{DS}$  and a voltage drop across the current sense resistor ( $V_{CS}$ ) and maximum  $I_{DS}$  current that can be provided by the current mirror.

If full  $V_{DS}$  voltage is applied to the current mirror, its current has maximum value, which is equal to  $I_{DS}/200$ . Decreasing this voltage to 54% of the  $V_{DS}$  due to high  $R_{CS}$  decreases  $I_{CS}$  to 40% of its expected value.

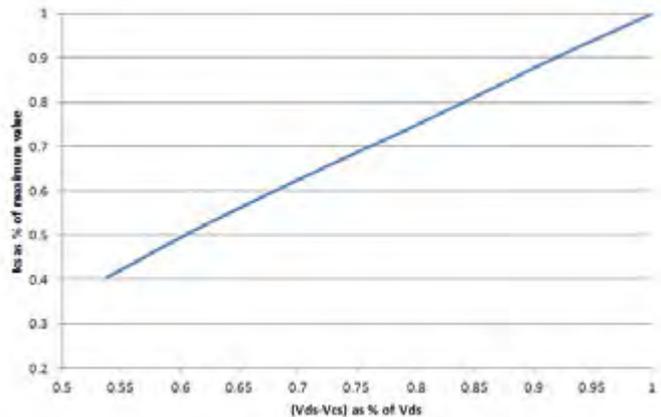


Figure 6: Utilizing Current Mirror's Current  $I_{CS}$  vs. Current Mirror's Head Room ( $V_{DS} - V_{CS}$ ) at  $I_{DS} = +10$  A

Therefore, a compromise between precision of measurement and signal level is required. High precision of the current measurement requires low value current sense resistors and signal amplifying, while low precision measurement may utilize high value current sense resistors at the expense of temperature dependency.

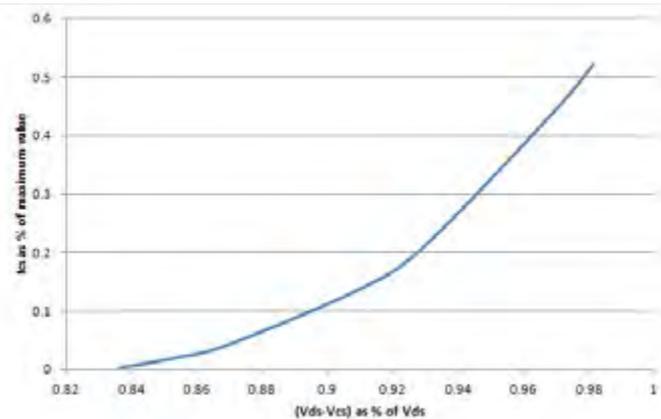


Figure 7: Utilizing Current Mirror's Current  $I_{CS}$  vs. Current Mirror's Head Room ( $V_{DS} - V_{CS}$ ) at  $I_{DS} = -10$  A

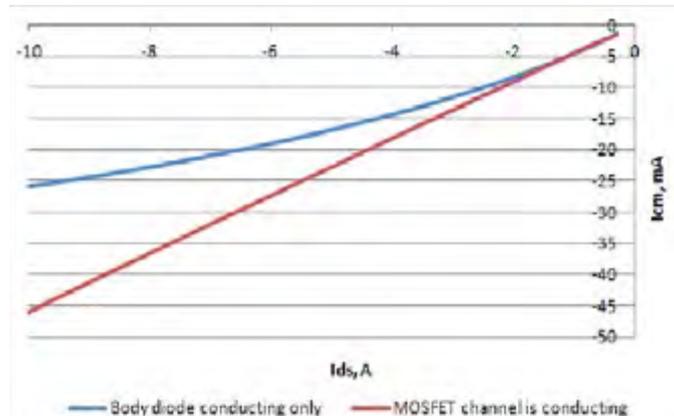


Figure 8:  $I_{CM}$  vs. Negative  $I_{DS}$  with MOSFET in ON and OFF States

**Current Mirror Behavior with Body Diode Active**

Figure 3 shows that when the MOSFET is in ON state and negative voltage is applied to the drain with respect to source, the channel

intercepts the entire current as long as the voltage drop across the channel is less than the body diode forward voltage and current is not flowing through the diode. In this case, the current mirror's behavior is the same as with positive current (see Figures 4 and 5).

However, if the MOSFET is in OFF state and negative voltage is applied to the drain with respect to source, the current mirror's behavior varies significantly from the expected behavior.

At first, the proportion between currents through the current mirror's body diode and major body diode is not equal to 1/200 as expected; instead, it is  $-0.52/200$ , i.e. two times less. This can be due to the current mirror's body diode utilizing significantly less silicon volume than that of the major body diode, resulting in higher resistance.

Further, as shown in Figure 7, ICM dependency from the current mirror's head room is not linear any longer, and without regard to relatively high head room voltage, current falls dramatically. Therefore, in this case, the current mirror's output primarily copies  $V_{DS}$ , determined by a major body diode's voltage drop. Even the highest head room voltage on the current mirror does not guarantee linearity between  $I_{DS}$  and  $I_{CS}$  currents, as shown in Figure 8.

Because of such behavior, the current mirror is not recommended for precise current measurements at negative  $I_{DS}$  currents, if the body diode is conducting. However, the signal from the current mirror can be used to trigger the gate driver to activate the MOSFET and connect the channel in parallel to the body diode. It significantly decreases the voltage drop on the MOSFET and improves efficiency at currents creating lower voltage drop on the channel than the body diode conducting voltage.

#### Current Mirror Behavior at High Negative Currents

Figure 9 shows the MMIXT132N50P3 drain/source voltage drop ( $V_{DS}$ ) as a function of the drain/source current ( $I_{DS}$ ) at currents up to -40 A, with currents flowing when drain is negative with respect to source (inverse connection) with the MOSFET in ON and OFF states.

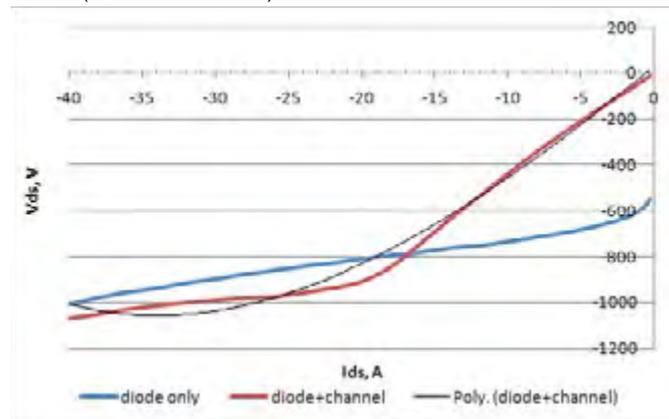


Figure 9:  $V_{DS}$  vs.  $I_{DS}$  at high negative currents

Legend: Red line - MOSFET is in ON state and channel is connected in parallel to the body diode

Blue line - MOSFET is in off state and body diode is conducting only

If the MOSFET is in ON state,  $R_{DS(on)}$  becomes function of  $I_{DS}$  at high negative currents. When absolute value of the drain/source voltage drop  $|V_{DS}|$  raises above 0.6 V, body diode starts conducting, which results in increased  $R_{DS(on)}$  value. As a result, interception of two curves appears earlier than we may expect based on steady  $R_{DS(on)}$  value at low currents, i.e. at -17 A instead of -20 A. Moreover, after

interception point, two structures (body diode and conducting channel) working in parallel results in higher  $V_{DS}$  voltage drop than if body diode is conducting only. At this region, body diode and MOSFET's channel cannot be interpreted as two independent structures like diode and resistor connected in parallel. It means that to get higher efficiency, MOSFET should be turned off after absolute value of the negative current goes above interception point.

Also, current mirror behavior in this region becomes very complex. Figure 10 shows the current mirror's current  $I_{CM}$  as function of the drain/source current  $I_{DS}$  with  $R_{CS} = 0.5 \Omega$ , and figure 11 shows utilization of the current mirror's current normalized to expected value of 1/200 of  $I_{DS}$ .

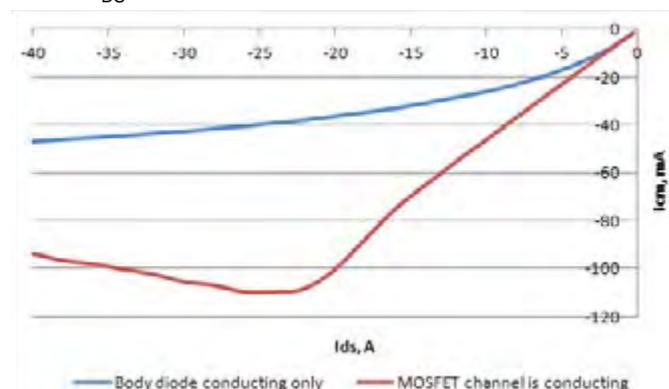


Figure 10:  $I_{CM}$  vs. Negative  $I_{DS}$  with MOSFET in ON and OFF States

$I_{CM}$  current lost linearity immediately after interception point at  $I_{DS} = -17$  A. Utilization of the ICM raises up to 1 immediately after that point and falls fast after that to the level determined mostly by a body diode. Using current mirror's current at  $|I_{DS}| > 17$  A for regulation or current monitoring purposes becomes problematic due negative current mirror's resistance, which may results in oscillations.

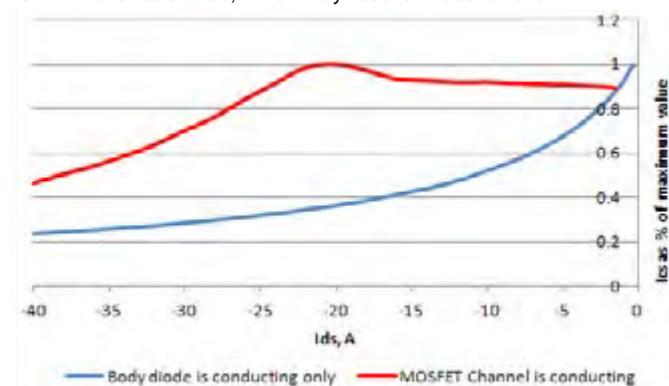


Figure 11: Utilizing Current Mirror's Current  $I_{CS}$  vs. Negative  $I_{DS}$

#### Current Mirror Application Schematic

Figure 12 depicts a typical application circuit for positive current measurement. It contains operational amplifier U1 with gain = 10 that allows converting of a 40 A drain/source current into a 2 V ADC input signal.

It is recommended that the A to D conversion be started with a ~600 ns delay time after the Q1 gate is activated to avoid errors related to gate charge current flowing through current sense resistor R1. Additionally, close attention should be paid to the PCB layout to avoid high source current flowing through signal ground traces. Signal and power ground traces should be kept connected at one point only at the source current output.

Figure 13 represents an application with a circuit that monitors cycle-by-cycle over-current conditions and turns the MOSFET off immediately upon occurrence of such conditions. It includes comparator U1 with a 64 mV threshold and 36 mV hysteresis, which has logic high output if voltage drop at current sense resistor does not exceed 100 mV. This circuit also includes trigger U3, gate driver U5, input buffer with Schmitt trigger U9, blanking time generator U6, U7, U8, and auxiliary logic U2, U4.

The device starts with a signal applied to the IN input, which sets the gate driver's U5 output high turning MOSFET Q1 on. Both channels of the driver U5 are used in parallel to increase the driver's current capability. Schmitt trigger U9 is used to improve input signal noise immunity.

If the drain/source current exceeds the comparator's threshold, which corresponds to  $I_{ds} = 14.8$  A, the comparator trips into logic low state that resets trigger U3 and aborts the input pulse which kept the MOSFET's Q1 gate high. When current falls below the comparator's threshold and the comparator's output becomes logic high again, trigger U3 output remains low until the next pulse is applied to the IN terminal.

Logic elements U6, U7, and U8 with the R8C3 network create a blanking time generator that keeps the comparator's output logic high for ~600 ns to finalize the transition process related to gate charge.

The drain/source current value at which current is interrupted can be adjusted by the current sense resistor value or comparator's threshold value, or both.

Figure 14 represents an application with a circuit that monitors negative current flowing through the MOSFET's body diode. It turns the MOSFET ON if the current exceeds the preset threshold, and switches it OFF, when it falls below this value. It includes comparator U1 with a 47 mV threshold and 34 mV hysteresis, which has logic low output if the absolute value of the voltage drop at current sense resistor does not exceed ~80 mV. This circuit also includes trigger U5, gate driver U10, input buffer with Schmitt trigger U11, blanking time generator U7, U8, U9, and auxiliary logic U2, U3, U4, and U6.

If a signal is applied to the IN terminal, the device operates as a standard gate driver regardless of the direction of the drain/source current setting gate driver's U10 output high and MOSFET Q1 ON state. Both channels of U10 are used in parallel to increase the

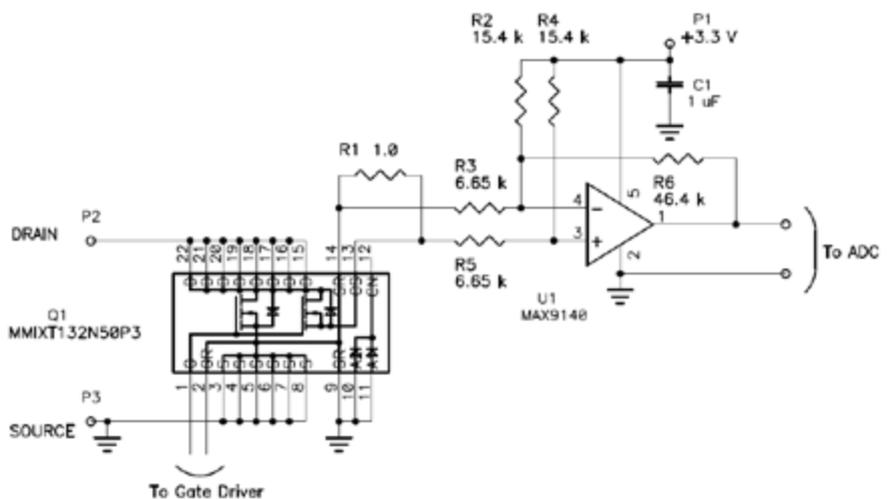


Figure 12: Positive Current Mirror Current Measurement Circuit

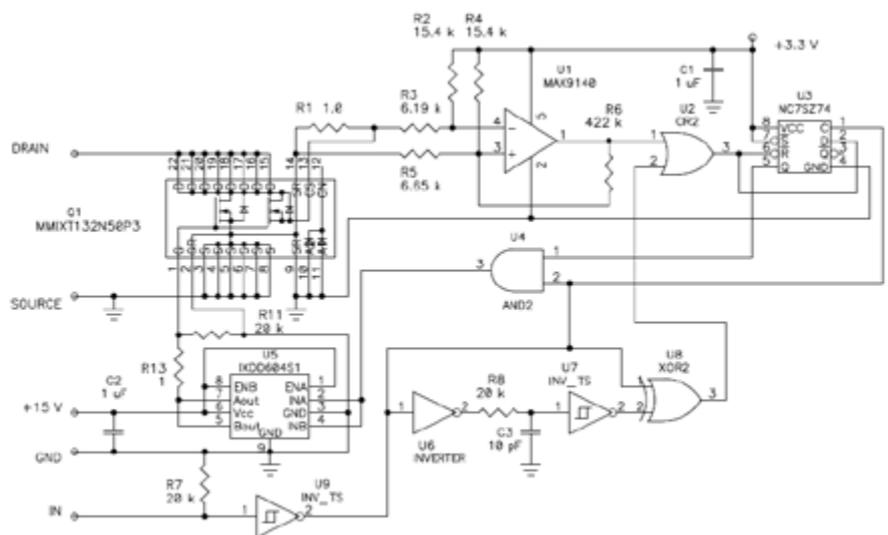


Figure 13: Positive Current Cycle-by-Cycle Overcurrent Monitoring System

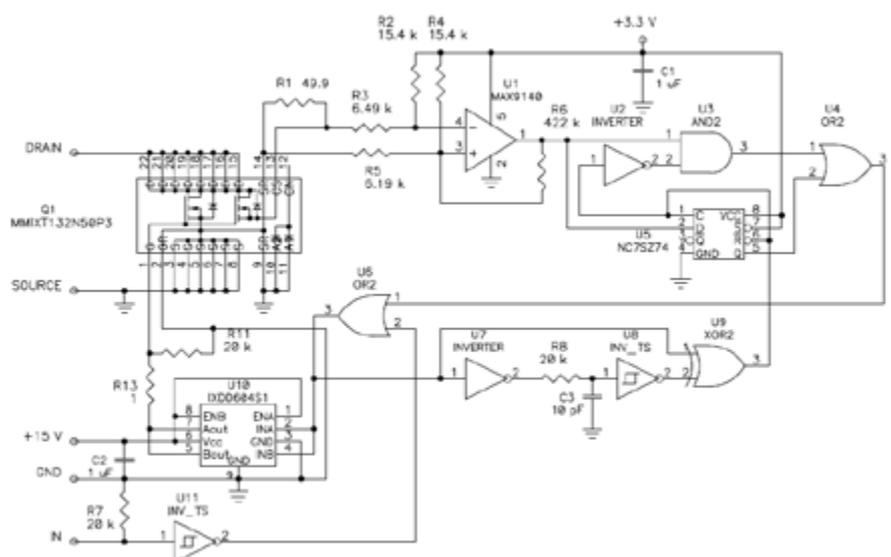


Figure 14: Negative Current (Body Diode Current) Monitoring System

driver's current capability. Schmitt trigger U11 is used to improve input signal noise immunity.

However, if no external signal is applied to the IN terminal and the MOSFET's body diode current exceeds the comparator's U1 threshold, its output goes logic high, activates the gate driver, and turns the MOSFET to ON state, connecting the MOSFET's channel in parallel to the body diode and reducing the drain/source voltage drop to increase efficiency.

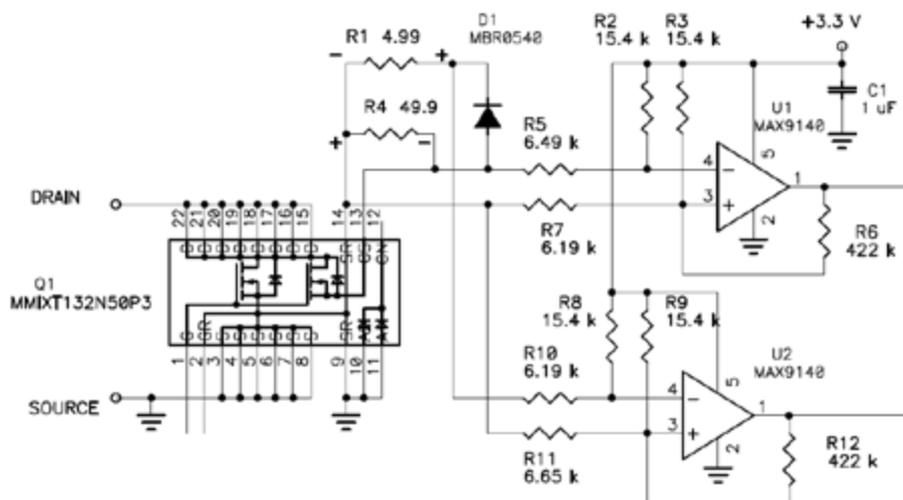


Figure 15: Separating Current Sense Resistors with Diode

When negative current falls below the comparator's U1 threshold, its output goes logic low, which turns gate driver U10 and the MOSFET OFF. After that, low negative current flows only through the body diode again. This allows for automatic turn on/off of the MOSFET in case it operates as a diode in motor drive circuits or buck converters without engaging special controllers to synchronize the input signal of the gate driver with actual diode current.

The comparator's threshold in this schematic corresponds to  $I_{ds} \sim -0.8$  A to turn the MOSFET on and  $\sim -0.4$  A to turn the MOSFET off. The threshold can be adjusted to another current value by changing current sense resistor R1 or the comparator's initial setting.

Logic elements U7, U8, and U9 with the R8C3 network create a blanking time generator that keeps the comparator's output logic level unchanged for  $\sim 600$  ns to finalize the transition process related to gate charge/discharge.

Using both positive and negative current comparators in the same design requires different current sense resistors to provide desired thresholds for positive and negative

currents. One possible solution is to separate current sense resistors with low forward voltage diode, as shown in Figure 15.

Current sense resistors R1 and R4 are separated by diode D1. For a negative current, only resistor R4 is used and its value determines the sensitivity to negative current. For a positive current, both resistors are connected in parallel with diode D1 in series with resistor R1. This creates some nonlinearity at low positive currents; however, it does not affect the area where positive current should

be limited. Figure 16 represents a voltage drop at current sense resistor R1 vs. drain/source current with  $R4 = 49.9$  ohm and  $R1 = 10$  ohm and  $R1 = 4.99$  ohm.

#### Temperature Measurement Diodes

Use diodes as temperature sensors based on the relatively high temperature coefficient of about  $0.2$  mV/°C, which is fairly linear.

The current flowing through the diode when it is forward biased is equal to [2]

$$I = I_s (e^{\frac{V}{\eta V_T}} - 1)$$

where  $I_s$  is the reverse saturation current,  $V$  is the diode's forward voltage drop,  $\eta$  is ideality factor (a constant which has a value ranging from 1 to 2),  $V_T = kT/q$  is the thermal voltage of the diode,  $T$  is the absolute junction temperature in Kelvin,  $q = 1.602 \times 10^{-19}$  C is the electron charge, and  $k = 1.38 \times 10^{-23}$  J/K is the Boltzmann's constant:

If a known current is flowing through the diode, its temperature can be determined as a function of the forward voltage drop as follows assuming that  $e^{\frac{V}{\eta V_T}}$ :

$$T = \frac{q}{k\eta} / \ln\left(\frac{I}{I_s}\right)$$



# Better safe than sorry!

## DC/DC Converters for IGBT & SiC

- Up to 6.4kVDC isolation
- Asymmetric outputs for IGBT & SiC
- Reinforced isolation
- 1W & 2W DC/DC converters
- UL / IEC / EN 62368-1 & UL / IEC / EN 60950 certified



# RECOM

WE POWER YOUR PRODUCTS

www.recom-power.com

This equation contains the reverse saturation current  $I_S$  and ideality factor  $\eta$ , which are part-dependent and should be determined before measurement.

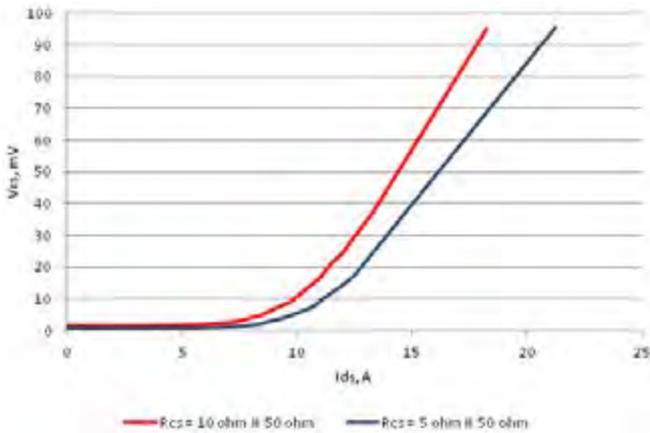


Figure 16: Voltage Drop at Current Sense Resistor vs. Drain/Source Current with Diode Separating Current Sense Resistors

If two known currents  $I_1$  and  $I_2$  are passed through the diode, or two identical diodes are used simultaneously, its temperature can be determined as

$$T = (V_2 - V_1) \frac{q}{k\eta} / \ln\left(\frac{I_2}{I_1}\right),$$

with  $I_S$  excluded from the equation.

If  $I_2/I_1 = 10$ , this equation simplifies to

$$T = (V_2 - V_1) \frac{q}{2.3k\eta} .$$

The MMIXT132N50P3 contains two identical diodes that can be used for temperature measurement, either in a single-ended or differential scheme. The recommended forward currents are 1 mA for a single-ended scheme and 1 mA and 100  $\mu$ A for a differential scheme with short pulses every 1–3 seconds. Higher, steady currents are not recommended to avoid self-heating of the diodes, which may create incorrect results.

**Application Schematic for Temperature Measurement**

Figure 17 shows a typical schematic diagram which is recommended for temperature measurement using two MMIXT132N50P3 integrated diodes. It contains two current sources generating stable currents. The first current source (U1:A, U2:1) generates 1 mA current, while the second current source (U1:B, U2:2) generates 100  $\mu$ A current. Variable resistor R5 provides the ability to adjust current from the first current source to obtain an exact 1:10 proportion. Voltage drop across diodes is measured by ADC

converters and used to calculate the die temperature of the MMIXT-132N50P3. IXYS recommends the use of the microcontroller unit's port as a 3.3 V voltage source to activate the circuit during temperature measurement only. Doing so helps prevent self-heating of the diodes, which can be a source of errors in temperature measurement.

**References**

1. MMIXT132N50P3 Data Sheet; IXYS Corporation. 2016
2. Andrei Grebennikov (2011). "§2.1.1: Diodes: Operational principle". RF and Microwave Transmitter Design. J Wiley & Sons. p. 59. ISBN 0-470-52099-X.

www.ixys.com

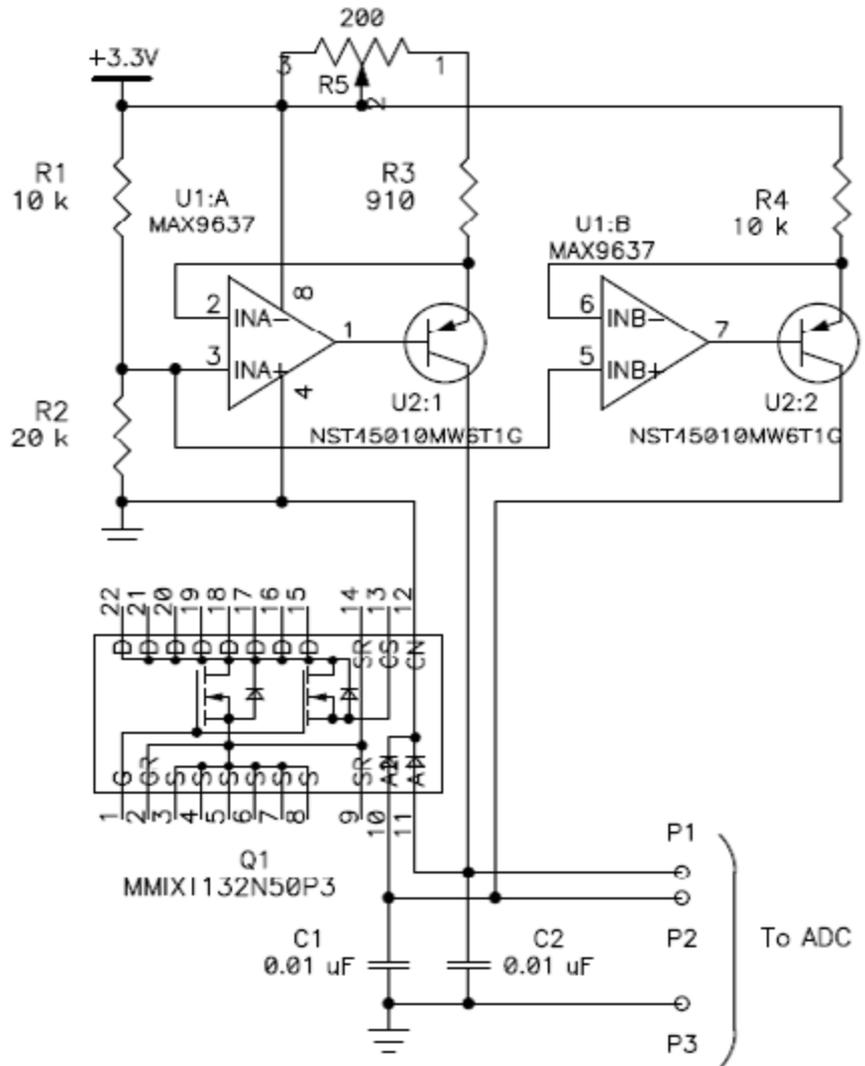


Figure 17: Typical Application Schematic for Temperature Measurement with Two Diodes